 


1. Introduction

In this lab you have to identify the critical path in your design (4-bit adder) and reduce the delay of this path by determining the optimal number of devices and sizes of the gates that lie along this path. You must use the Logical Effort and Gate sizing techniques you learn in the course.

2. Design **transistor level** schematic for 4-bit adder


Attached is a sample of the transistor level schematic of the 4-bit adder and its critical path. It is unwise to use symbols for nand/xor/1-bit adder. The reason is any changes made to any of the nand/xor/1-bit adder schematic will also be saved on other nand/xor/1-bit adders. For this reason, you need to draw the transistor level of the 4-bit adder to keep each gate independent from the others.



Second, please identify the critical path on your schematic by screenshot the schematic and draw a line along the critical path. The critical path is a logical path from an input pin to an output pin on your circuit that involves most logic gates. In the sample above, the critical path starts from one XOR2 and goes through 8 NAND2.

Complete the following calculation process of logical effort optimization.

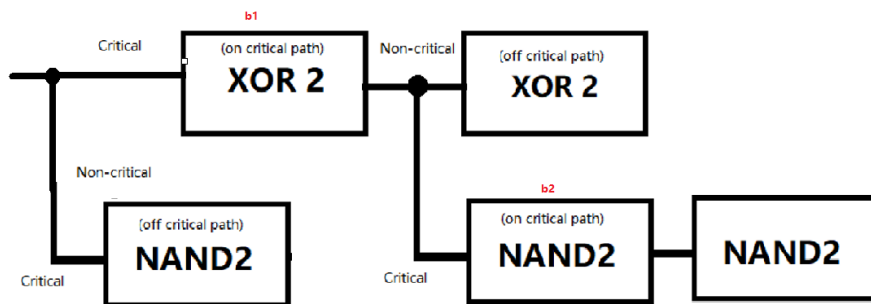- For example, $b_1 = (C_{xor} + C_{nand2}) / C_{xor}$, $b_{2,4,6,8} = (C_{xor} + C_{nand2}) / C_{nand2}$, $b_{3,5,7,9} = 1$ (since there is no branch, $C_{off_critical_path} = 0$)



- If $2.7 < \hat{f} < 4$, perform the following resizing:
For the i-th gate, $i = 9, 8, 7, \dots, 1$, calculate: $C_{in,i} = g_i C_{out,i} / \hat{f}$
(Resize from the last nand gate.)
- If $C_{in,i} < C_{gate}$, keep the size (New sizes should always grater or equal to old sizes.). Otherwise resize the i-th gate by $C_{in,i} / C_{gate}$ times the old size.
For instance, if a nand gate needs to be resized by the value of 1.2, the width (Wn and Wp) of all 4 transistors in that gate should be modified with the same ratio. Resizing is done on the schematic level and only applied to the width (not length). There is no layout in this lab, update the sizes in your lab 9 schematic only.

3 Report Requirements

- Include your transistor level schematic and draw a line on it to indicate the critical path.
- Please report 4 optimized pre-layout simulation waveforms for the following in-put vectors:

A=0000, B=1111, CarryIn=1:

A=1010, B=0101, CarryIn=0:

A=1010, B=0101, CarryIn=1:

A=1100, B=1000, CarryIn=0:

And complete the following tables:

Delays:

Case	Pin	Non-optimized (ps)	Optimized (ps)
A=0000 B=1111 Carry In=1	SUM.0		
	SUM.1		
	SUM.2		
	SUM.3		
	CARRY		
A=1010 B=0101 Carry In=0	SUM.0		
	SUM.1		
	SUM.2		
	SUM.3		
	CARRY		
A=1010 B=0101 Carry In=1	SUM.0		
	SUM.1		
	SUM.2		
	SUM.3		
	CARRY		
A=1100 B=1000 Carry In=0	SUM.0		
	SUM.1		
	SUM.2		
	SUM.3		
	CARRY		

Power consumptions:

Case	Optimized (uW)	Non-optimized (uW)
A=0000, B=1111, CarryIn=1		
A=1010, B=0101, CarryIn=0		
A=1010, B=0101, CarryIn=1		
A=1100, B=1000, CarryIn=0		

Area:

Optimized (μ^2m^2)	Non-optimized (μ^2m^2)

Area is the sum up all the transistors' W*L.

Lab 9 Rubric:

1. Circuit with critical path (0.5)
2. Calculate G, B, H and attach the calculation procedure (0.5*3)
3. Resizing procedure & transistors' sizes (1.5)
4. Waveforms (0.5*4)
5. Table comparing delays and VDD power consumption (0.5*4, 0.5*4)
6. Table comparing area (0.5)